

# Computer Organisation and Architecture Lab


Group number: 65

Members: Pranav Mehrotra ( 20CS10085)

Saransh Sharma (20CS30065)

## Q1) RCA using Verilog


### i.) Half Adder

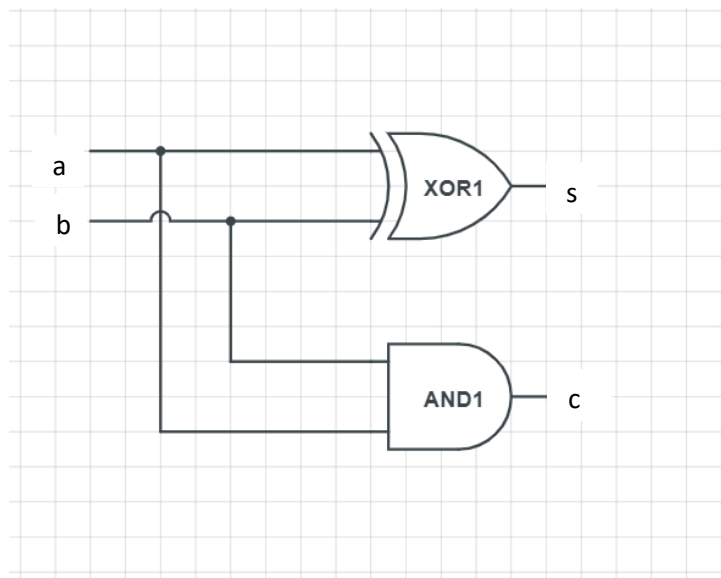

**Truth Table of a Half Adder**


Input		Output	
A	b	s (Sum)	c (carry)
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

## ii.) Full Adder

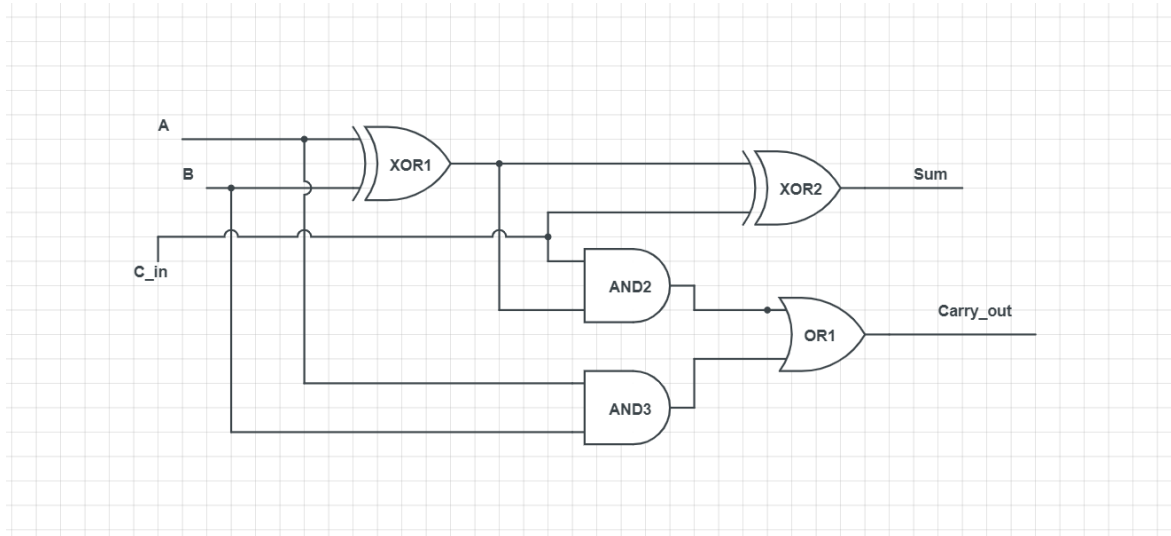


Truth Table of a Full Adder				
Input			Output	
A	B	C <sub>in</sub>	Sum	Carry_out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


### iii.) 8 – Bit Ripple Carry Adder

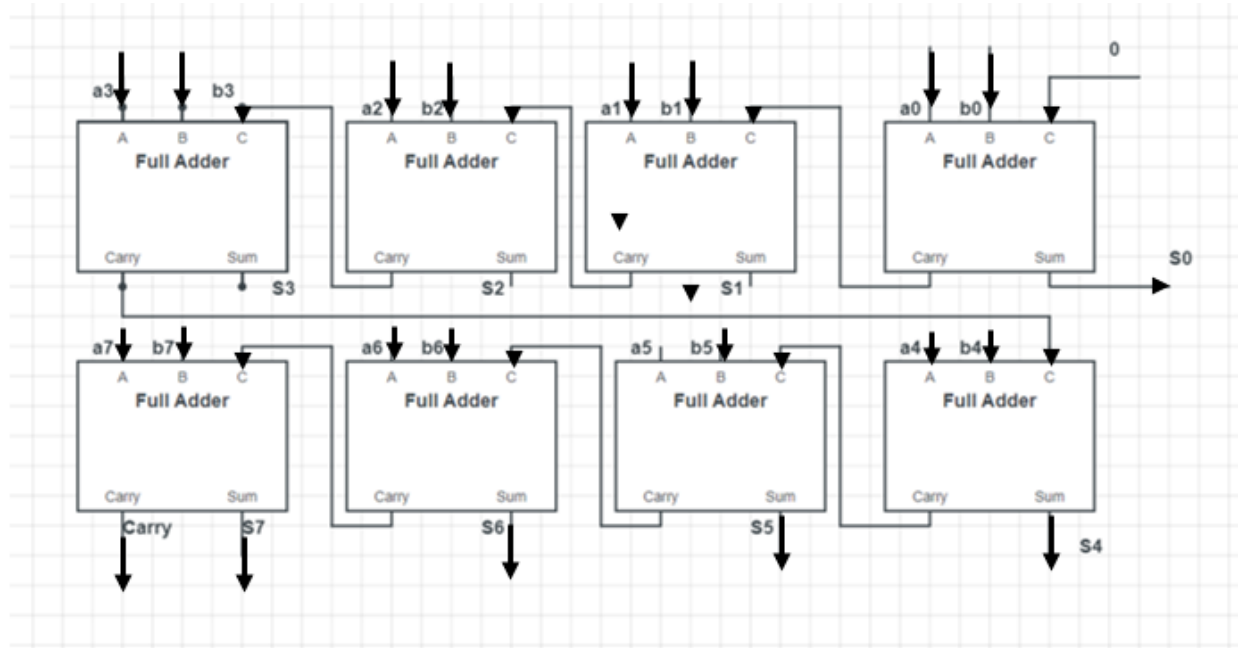


### iv.) 16- Bit RCA

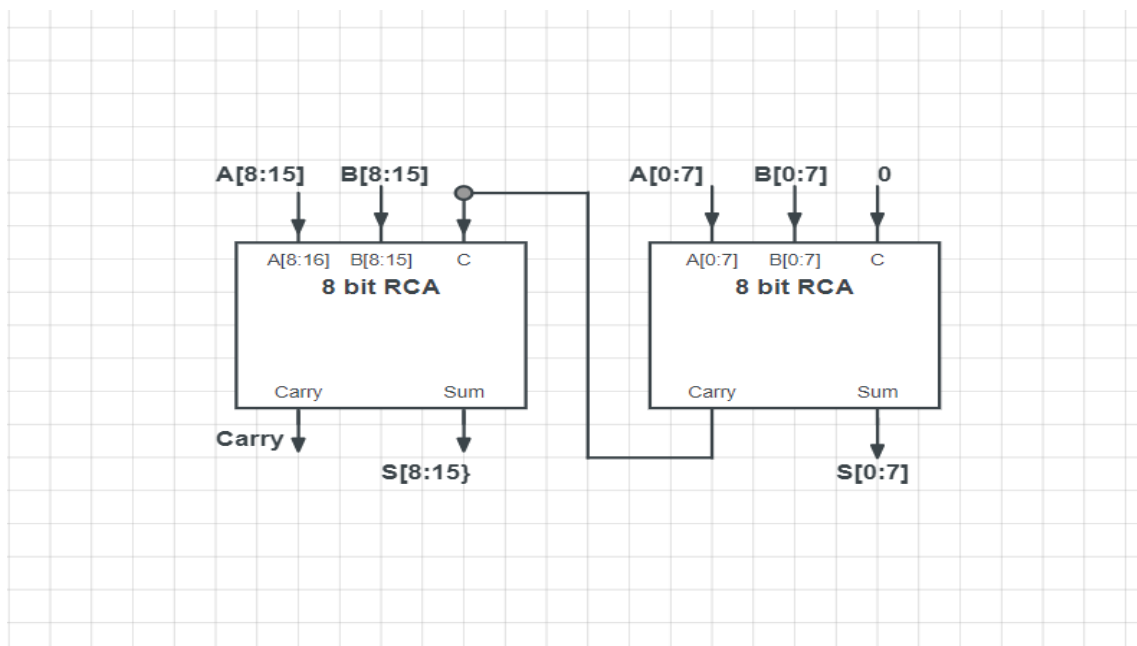

v.) 32-Bit RCA

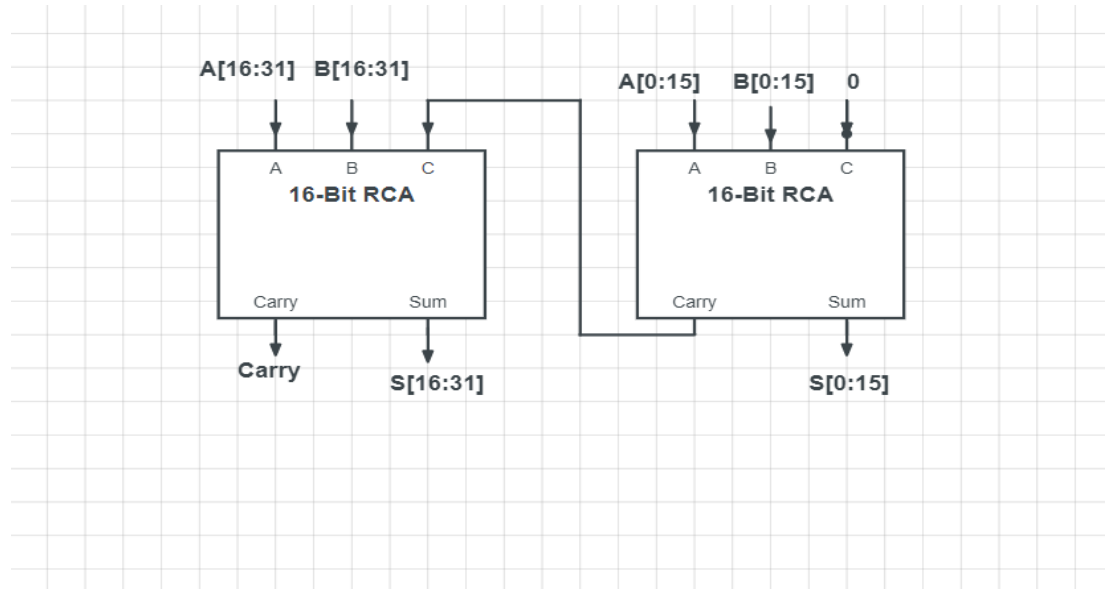

vi.) 64- Bit RCA

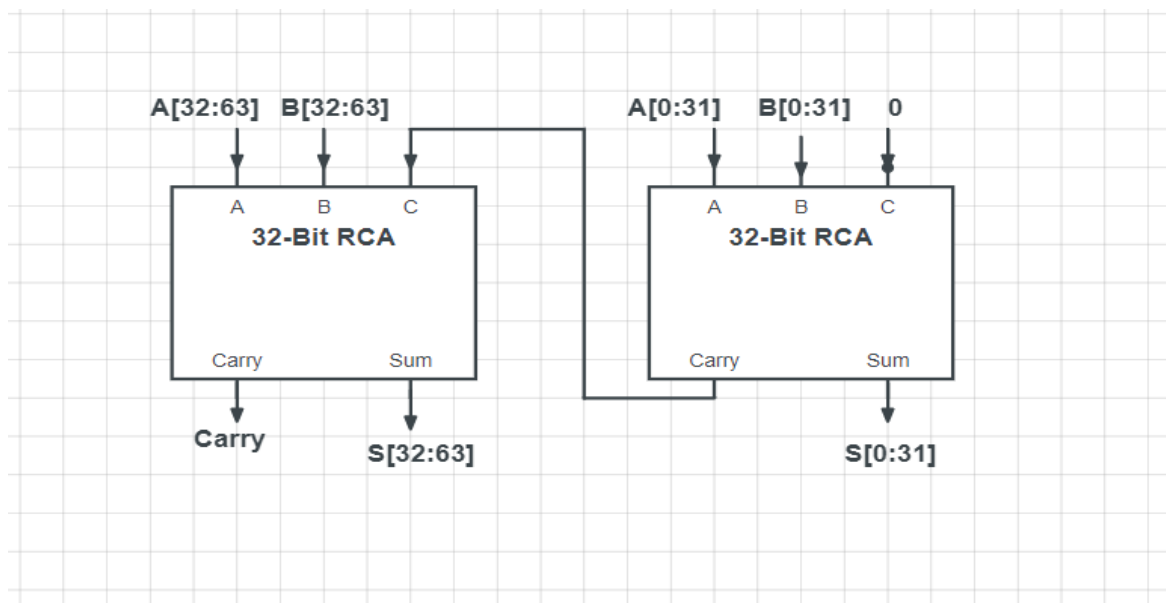

Question: How can you use the above circuit, to compute the difference between two n-bit numbers?

Answer: Ripple Carry adder with input a and b and initial carry bit  $c_0$  actually computes the binary sum of a and b, also adding  $c_0$  to the LSB of the sum. Thus,  $c_0$  is set to 0 so that RCA adds a and b bitwise and output the result.

For finding difference between two number a and b i.e.,  $a-b$  we will convert the subtraction problem into addition problem:

$$\text{i.e., } a - b = a + (-b) \text{ where } (-b) \text{ is the 2's complement of } b.$$

we know that 2's complement of any number can be calculated by computing 1's complement of that number and then adding 1 to the LSB of the 1's complement. That is,  $(-b) = (\sim b) + 1$  where  $(\sim b)$  is the 1's complement of b

$$\text{let } a = 100 \text{ (4) and } b = 010 \text{ (2) and } n=3$$

$$\text{therefore, } a - b = 100 - 010$$

$$-b = 101 (= \sim b) + 1 = 110$$

$$a - b = 100 + (110) = 010 \text{ (carry\_out = 1)}$$

To calculate 1's complement of a number, we simply have to flip all the bits of that number. That is, we pass every bit of b to a NOT gate to flip the bits of the b. Therefore, whenever we need to calculate difference between a and b i.e.,  $a-b$  we would first calculate 1's complement of b by taking NOT of every bit of b with 1. Since we also need to add 1 to the 1's complement calculated, we would pass this 1 as  $c_0$  to the RCA. Therefore, upon passing a,  $(\sim b)$  and 1 as input to RCA, the n-bit RCA can calculate the difference between a and b.

## Synthesis Report

Circuit	Delay (in ns)	Logic Levels	Number of Slice LUTs	Number of bonded IOBs
Half Adder	1.066	3	2	4
Full Adder	1.246	3	2	5
8-Bit RCA	3.471	6	12	26
16-Bit RCA	6.167	10	24	50
32-Bit RCA	11.559	18	48	98
64- Bit RCA	22.343	34	96	194

## Part-2 Carry Look- Ahead Adders

### 1. 4- Bit Carry Look-Ahead Adder

The prominent difference between a 4-Bit RCA and a 4- Bit CLA is that a CLA calculates all carries simultaneously instead of waiting for the carry from the previous block to be passed to the current block, thereby, reducing the delay in calculation of sum.  $C_i$  that is carry when  $i$ th bit of inputs is added can be represented in the form of  $C_0$  (initial carry bit).

The logic for CLA for 2 4-Bit input X and Y is shown as:

$$G[i] = X[i] \& Y[i]$$

$$P[i] = X[i] \oplus Y[i]$$

Where  $G_i$  denotes whether  $X[i]$  and  $Y[i]$  upon addition generate a carry on their own and  $P_i$  denotes whether the carry from previous block will be propagated forward or not.

Let  $C_0$  be the initial input carry bit.

$$\text{Sum}[i] = P[i] \oplus C[i]$$

$$C[i+1] = G[i] + P[i]C[i]$$

(Notation:  $A \& B \rightarrow AB$  and  $A \text{ or } B \rightarrow A + B$ )

Upon further expanding


$$C[1] = G[0] + P[0]C[0]$$

$$C[2] = G[1] + P[1]G[0] + P[1]P[0]C[0]$$

$$C[3] = G[2] + P[2]G[1] + P[2]P[1]G[0] + P[2]P[1]P[0]C[0]$$

$$C[4] = G[3] + P[3]G[2] + P[3]P[2]G[1] + P[3]P[2]P[1]G[0] + P[3]P[2]P[1]P[0]C[0]$$

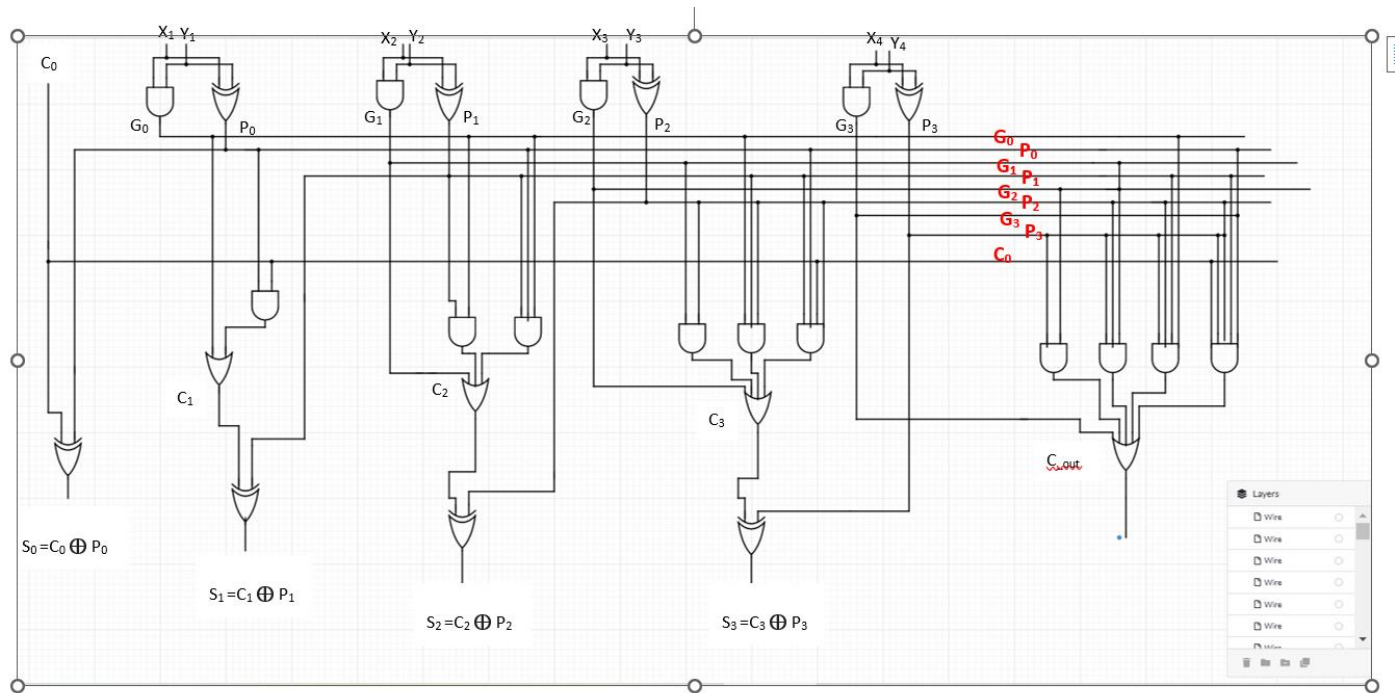That is all  $C[1]$ ,  $C[2]$ ,  $C[3]$ ,  $C[4]$  can now be represented in terms of  $C[0]$ .



## 2. 4-Bit Carry Look Ahead Adder (augmented)

The previous circuit will be modified so that the block outputs propagate P and generate G instead of carry-out. This P and G will help us in constructing 16-Bit and higher order CLA using 4-Bit CLA.


The expressions of  $C[i]$  and  $\text{Sum}[i]$  remains the same, i.e.,

$$\text{Sum}[i] = P[i] \oplus C[i]$$

$$C[i+1] = G[i] + P[i]C[i]$$


$$P = P[3]P[2]P[1]P[0]$$
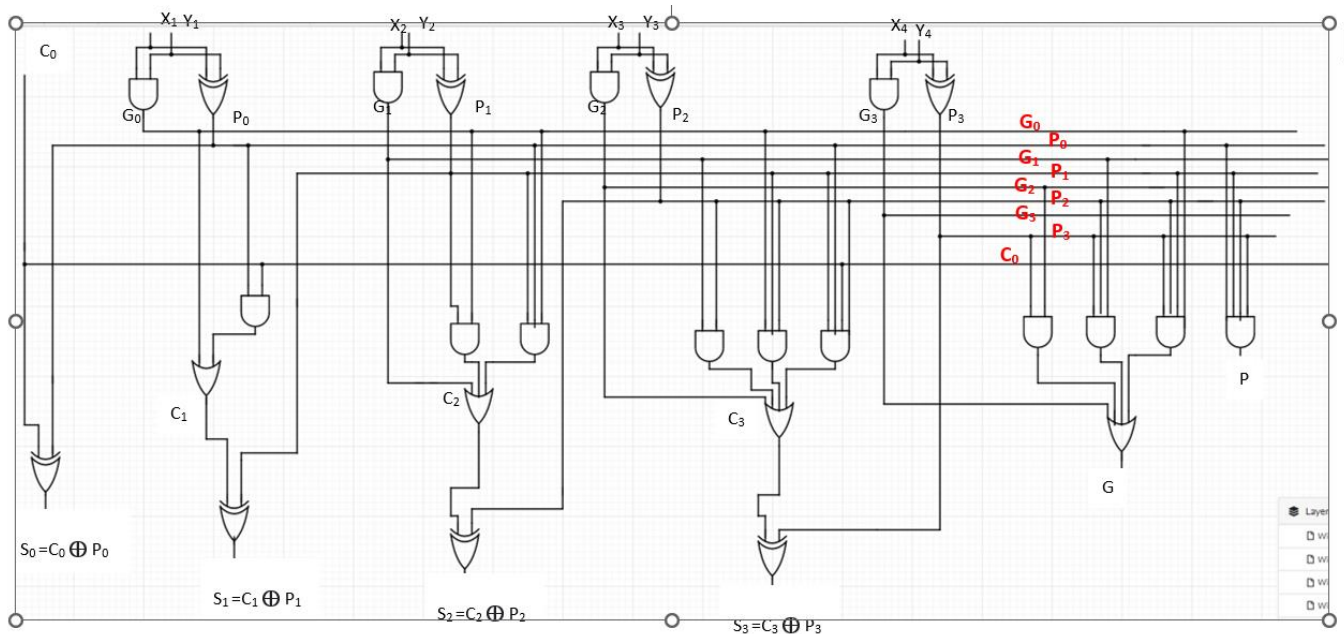
$$G = G[3] + P[3]G[2] + P[3]P[2]G[1] + P[3]P[2]P[1]G[0] + P[3]P[2]P[1]P[0]C[0]$$


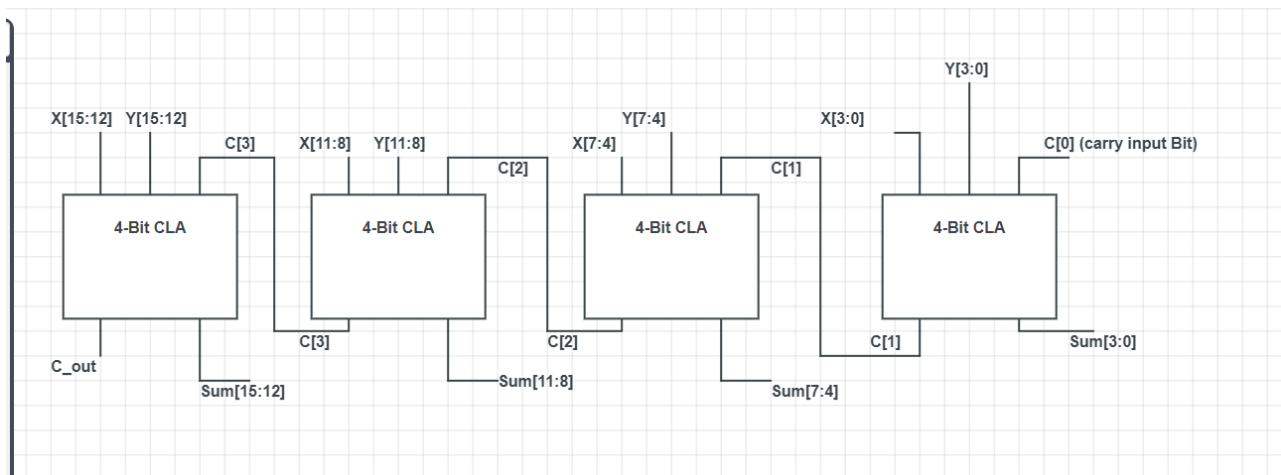
### 3. 16-Bit Carry Look-Ahead Adder

16-Bit CLA can be constructed by connecting 4 4-Bit CLA and rippling the carry of one block to the next block.  $C[3]$ ,  $C[2]$  and  $C[1]$  are the internal carries of the circuit.



### 4. 16- Bit Carry Look- Ahead Adder (Look- Ahead Carry Unit)

The previous circuit has to wait for carry from previous block to do further calculations. We can reduce this delay by using an additional look-ahead unit along with 4 CLA's which can calculate carries using propagate and generate of the 4 CLA's. let  $P[0], P[1], P[2], P[3]$  be the propagates of the 4 blocks of CLA and  $G[0], G[1], G[2], G[3]$  be the generates of the 4 blocks of CLA. Using this 16-Bit CLA, delay is further reduced and this circuit can be then used for constructing higher order CLA's.



Equations involved:

$C_0$  is the input carry

$$\text{Sum}[i] = P[i] \oplus C[i]$$

$$C[i+1] = G[i] + P[i]C[i]$$

$$C[1] = G[0] + P[0]C[0]$$

$$C[2] = G[1] + P[1]G[0] + P[1]P[0]C[0]$$


$$C[3] = G[2] + P[2]G[1] + P[2]P[1]G[0] + P[2]P[1]P[0]C[0]$$

$$C[4] = G[3] + P[3]G[2] + P[3]P[2]G[1] + P[3]P[2]P[1]G[0] + P[3]P[2]P[1]P[0]C[0]$$

Also propagate and generate of this circuit would be:

$$P = P[3]P[2]P[1]P[0]$$
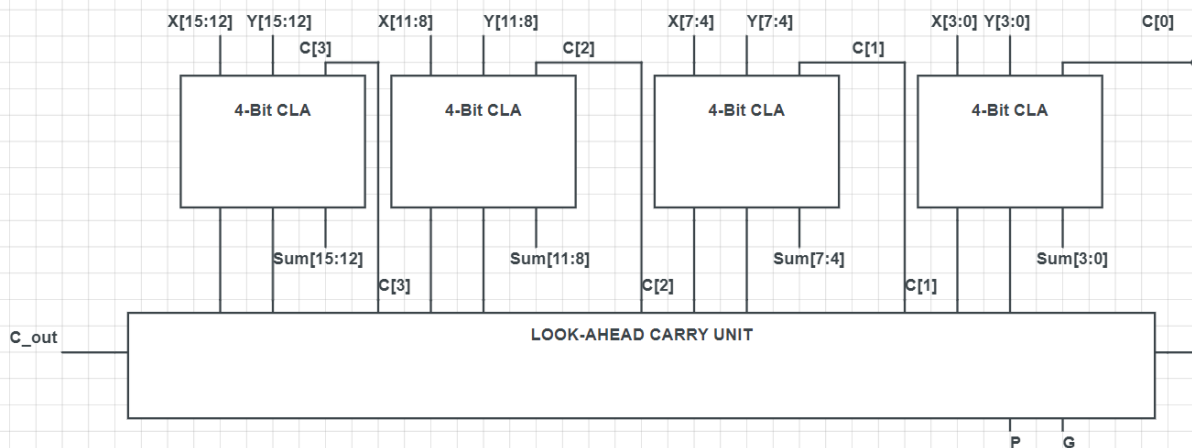
$$G = G[3] + P[3]G[2] + P[3]P[2]G[1] + P[3]P[2]P[1]G[0] + P[3]P[2]P[1]P[0]C[0]$$



## Synthesis Report

Component	Logic Delay	Route Delay	Total Delay (in ns)	Number of Slice LUTs	Logic Levels	Number of bonded IOBs
4-Bit RCA	0.497	2.697	3.194	8	10	14
4-Bit CLA	0.249	1.874	2.123	6	4	14
4-Bit CLA (augmented)	0.249	2.114	2.363	9	4	15
Look Ahead Carry Unit	0.373	2.623	2.996	7	5	15
16-Bit RCA	0.993	5.174	6.167	24	10	50
16-Bit CLA (with LCU)	0.745	4.563	5.30	43	11	52
16-Bit CLA (Ripple)	0.993	5.174	6.167	24	14	50